



Secure Sequence Recognizer

Author: Iacopo Pacini

Index

1Introduction.....	3
2Architecture.....	4
State Diagram.....	5
3Code.....	7
Secure Sequence Recognizer.....	7
Counter	12
4Test_benches.....	13
Correct sequence Testbench.....	13
Wrong sequence Testbench.....	15
5Synthesis on Vivado.....	17
Resource utilization.....	17
Critical path.....	18
Warnings.....	18

1 Introduction

A Secure Sequence Recognizer is a Mealy sequential state machine(In a Mealy machine, output depends on the present state and the external input).

It can detect the beginning of a packet of asynchronous data, like that coming in over wireless or a serial port. Can be used in a remote control application too, such as for a TV or garage door opener.


The device implemented is a synchronous sequence recognizer, the sequence numbers are five 8-bit integers. At the beginning of the process the signal must be set to '1' for one clock cycle and the following must be send to the SSR at the rate of 1 clock cycle.

The “first” pin must be kept high for no more than 1 clock cycle otherwise the SSR stops working until a future reset.

The sampling duration is always five clock cycles long and at the end the pin “unlock” is kept high for one clock cycle if the sequence has been inserted correctly.

Instead,if there is at least a wrong number in the sequence the pin “warning” goes to '1' for a clock cycle.

If it is being inserted a wrong sequence more than three times consecutively the SSR stops working and “warning” goes to '1' permanently or at least until the input pin “reset” goes to '0'

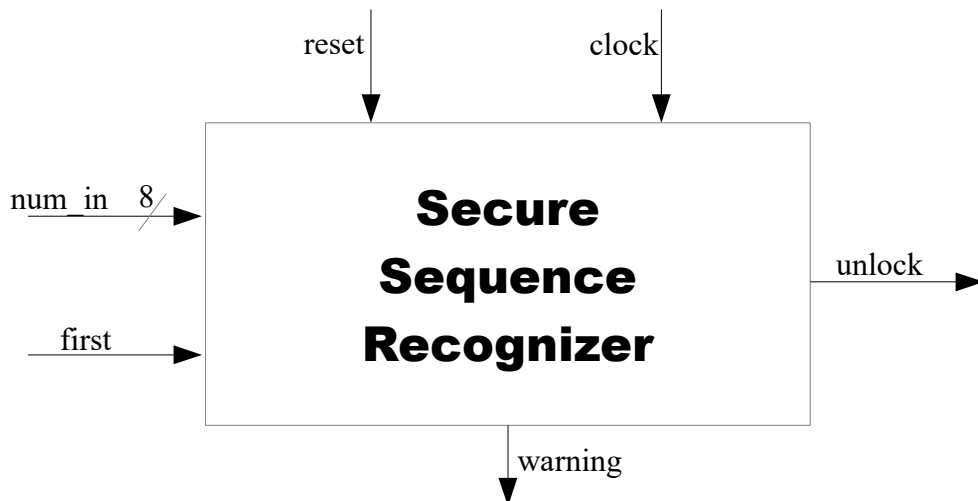

Picture 1: An I/O view of the device

2 Architecture

The SSR is a finite state machine whose state is described in the STAR register, the latter is a 3-bit register and the possible states are:


- 1) **SINIT**: the SSR in this state waits for the first sequence number and enters this state whenever the pin “reset” goes to '1'
- 2) **S0,S1,S2,S3,S4**: In each of those states the SSR samples the input sequences and checks for their correctness
- 3) **S5**: In this state the “unlock” pin is set to '1' if there were no input errors otherwise the 'warning' pin goes to '1' for a clock cycle.
- 4) **SBLOCK**: The SSR enters this state whenever the 'first' pin is kept high too long or in the wrong moment and if the sequence is inserted incorrectly for at least three consecutive times. The device leaves this state only if the 'reset' becomes high.

Some other tools are needed in order to make a correct sampling:

- **OK.**: 1-bit register that contains 1 if until now the sequences are correct, otherwise 0.
- **lut_seq**: Lookup table that contains the correct sequence.
- **SEQNUMBER**: 3-bit counter that drives the input of lut_seq.
- **COUNT_WRONG**: 2-bit counter that counts the number of consecutive wrong inputs.

State Diagram

Picture 2: SSR State diagram

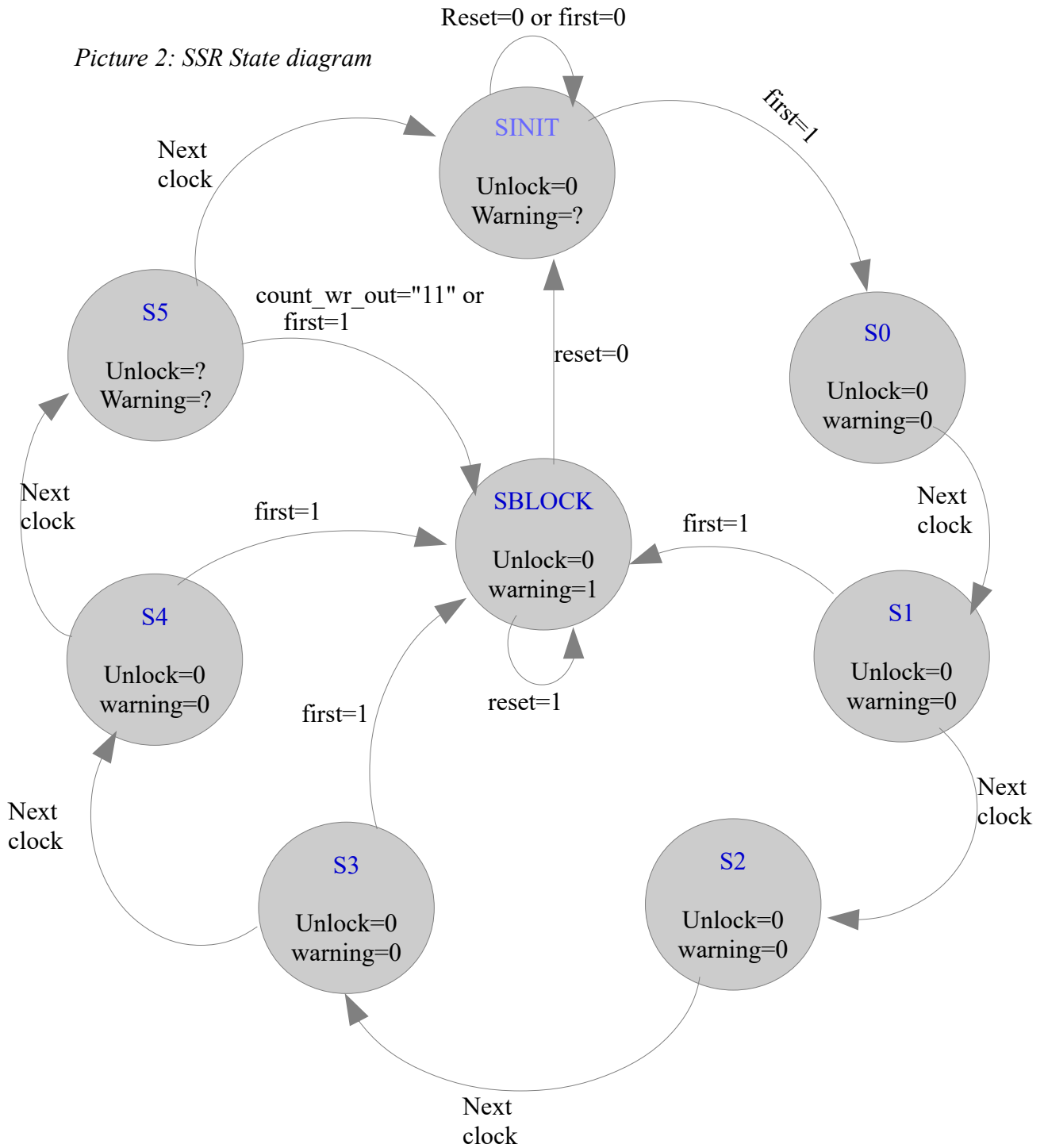

3 Code

Secure Sequence Recognizer

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;

entity SecureSequenceRec is
port (
    clock: in std_logic; --- clock signal
    reset: in std_logic; -- reset signal active low
    first: in std_logic; -- start sampling signal
    num_in: in std_logic_vector(7 downto 0); --input sequence number

    unlock: out std_logic; -- signal of success
    warning: out std_logic -- error signal
);
end SecureSequenceRec;

architecture SSR_beh of SecureSequenceRec is
    SUBTYPE STATE_TYPE_COUNT is STD_LOGIC_VECTOR (1 DOWNT0 0) ;
    CONSTANT SMEM: STATE_TYPE_COUNT := "00"; -- when in this state the counter just
    keeps the exit constant
    CONSTANT SINC: STATE_TYPE_COUNT := "01"; -- when in this state the counter
    increments the exit
    CONSTANT SRES: STATE_TYPE_COUNT := "11"; -- when in this state the counter
    keeps the exit equals to zero

    SUBTYPE STATE_TYPE is STD_LOGIC_VECTOR (2 DOWNT0 0) ;
    -- constants to drive the state
    CONSTANT SINIT: STATE_TYPE := "000";
    CONSTANT S0: STATE_TYPE := "001";
    CONSTANT S1: STATE_TYPE := "010";
    CONSTANT S2: STATE_TYPE := "011";
    CONSTANT S3: STATE_TYPE := "100";
    CONSTANT S4: STATE_TYPE := "101";
    CONSTANT S5: STATE_TYPE := "110";
    CONSTANT SBLOCK: STATE_TYPE := "111";

    signal signal_star_in : STATE_TYPE;
    signal signal_star_out : STATE_TYPE;

    signal lut_in : std_logic_vector(2 downto 0);
    signal lut_out : std_logic_vector(7 downto 0);

    signal signal_ok_in : std_logic_vector(0 downto 0);
    signal signal_ok_out : std_logic_vector(0 downto 0); -- 0 when a wrong number is inserted
```

```

signal count_wr_in : STATE_TYPE_COUNT; -- count the wrong sequences
signal count_wr_out : std_logic_vector(1 downto 0);

```

```

signal counter_state_in : STATE_TYPE_COUNT;

```

```

component DFF is

```

```

    generic(N_bit : integer);
    port (
        clk: in std_logic;
        reset: in std_logic;
        D: in std_logic_vector(N_bit-1 downto 0);
        Q: out std_logic_vector(N_bit-1 downto 0)
    );

```

```

end component;

```

```

component LUT is

```

```

    port(
        address : in STD_LOGIC_VECTOR(2 downto 0);
        data : out STD_LOGIC_VECTOR(7 downto 0)
    );

```

```

end component;

```

```

component Counter_mod is

```

```

generic(N_bitc : integer);
port(
    count_clk      : in      STD_LOGIC;
    count_reset    : in      STD_LOGIC;
    enabler_in     : in      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
    D_out          : out      STD_LOGIC_VECTOR(N_bitc-1 downto 0)
);

```

```

end component;

```

```

begin

```

```

OK: DFF --1 if the seq number is correct, 0 otherwise

```

```

generic map(N_bit => 1)
port map(clock,reset,signal_ok_in,signal_ok_out);

```

```

STAR: DFF --status register

```

```

generic map(N_bit => 3)
port map(clock,reset,signal_star_in,signal_star_out);

```

```

SEQNUMBER: counter_mod --Drives the lut

```

```

generic map(N_bitc => 3)
port map(clock,reset,counter_state_in,lut_in);

```

```

COUNT_WRONG: counter_mod --Keeps track of the wrong sequences

```

```

generic map(N_bitc => 2)
port map(clock,reset,count_wr_in,count_wr_out);

```

lut_seq : LUT *--contains the sequence numbers*

port map(lut_in,lut_out);

LOGIC:**process**(signal_star_out,reset,first)

begin

if(reset='0') **then**

signal_star_in<=SINIT;

unlock<='0';

warning<='0';

signal_ok_in<="0";

counter_state_in<=SRES;

count_wr_in<=SRES;

else

case(signal_star_out) **is**

when SINIT=> *-- the SSR in this state waits for the first sequence*

number

unlock<='0';

if(first='1') **then**

signal_star_in<=S0;

counter_state_in<=SINC; *--start counting*

else

signal_star_in<=SINIT;

counter_state_in<=SMEM;

end if;

warning<='0';

count_wr_in<=SMEM;

signal_ok_in<="0";

when S0 =>

count_wr_in<=SMEM;

unlock<='0';

warning<='0';

signal_star_in<=S1;

if(num_in = lut_out) **then** *--Checking Sequence number 0*

signal_ok_in<="1";

else

signal_ok_in<=signal_ok_out;

end if;

counter_state_in<= SINC;

when S1 =>

unlock<='0';

warning<='0';

count_wr_in<=SMEM;

if(first='1')**then** *--From now on it is an error if first goes to '1'*

and the device is being blocked

signal_ok_in<="0";

signal_star_in<=SBLOCK;

else

1

```

        if(num_in = lut_out)then --Checking Sequence number

            signal_ok_in<=signal_ok_out;
        else
            signal_ok_in<="0";
        end if;
        signal_star_in<=S2;
    end if;
    counter_state_in<= SINC;
when S2=>
    unlock<='0';
    warning<='0';
    count_wr_in<=SMEM;
    if(first='1')then
        signal_ok_in<="0";
        signal_star_in<=SBLOCK;
    else
        if(num_in = lut_out)then --Checking Sequence number

```

2

```

            signal_ok_in<=signal_ok_out;
        else
            signal_ok_in<="0";
        end if;
        signal_star_in<=S3;
    end if;
    counter_state_in<= SINC;
when S3=>
    unlock<='0';
    warning<='0';
    count_wr_in<=SMEM;
    if(first='1')then
        signal_ok_in<="0";
        signal_star_in<=SBLOCK;
    else
        if(num_in = lut_out)then --Checking Sequence number

```

3

```

            signal_ok_in<=signal_ok_out;
        else
            signal_ok_in<="0";
        end if;

        signal_star_in<=S4;
    end if;
    counter_state_in<= SMEM;
when S4=>
    unlock<='0';
    warning<='0';
    count_wr_in<=SMEM;
    if(first='1')then
        signal_ok_in<="0";
        signal_star_in<=SBLOCK;
    else

```

```

        if(num_in = lut_out)then --Checking Sequence number
            signal_ok_in<=signal_ok_out;
        else
            signal_ok_in<="0";
        end if;
        signal_star_in<=S5;
    end if;
    counter_state_in<= SRES;
when S5 =>
    unlock<= signal_ok_out(0);
    warning <= not signal_ok_out(0);
    if(signal_ok_out(0)='1') then
        count_wr_in<=SRES;
    else
        count_wr_in<=SINC;
    end if;
    counter_state_in<= SRES;
    if(first='1' or (signal_ok_out(0)='0' and count_wr_out="10" ))
then
        signal_star_in<=SBLOCK;
    else
        signal_star_in<=SINIT;
    end if;
    signal_ok_in<="0";
when SBLOCK=>
    unlock<='0';
    warning<='1';
    signal_star_in<=SBLOCK; --Blocking the SSR until a reset
event happens
        counter_state_in<= SRES;
        count_wr_in<=SRES;
        signal_ok_in<="0";

when others => -- avoiding unexpected behaviour due to bad driving
of the inner state
    unlock<='0';
    warning<='1';
    signal_star_in<=SBLOCK; --Blocking the SSR until a reset
event happens
        counter_state_in<= SRES;
        count_wr_in<=SRES;
        signal_ok_in<="0";

    end case;
end if;
end process;

end SSR_beh;

```

Counter

library IEEE;

use IEEE.std_logic_1164.all;

entity Counter_mod **is**

generic(N_bitc : integer);

port(

 count_clk : **in** STD_LOGIC;

 count_reset : **in** STD_LOGIC;

 enabler_in : **in** STD_LOGIC_VECTOR(1 **DOWNTO** 0) ;

 D_out : **out** STD_LOGIC_VECTOR(N_bitc-1 **downto** 0)

);

end Counter_mod;

architecture Counter_beh **of** Counter_mod **is**

SUBTYPE STATE_TYPE **is** STD_LOGIC_VECTOR (1 **DOWNTO** 0) ;

CONSTANT SMEM: STATE_TYPE := "00"; -- when in this state the counter just keep the
 exit constant

CONSTANT SINC: STATE_TYPE := "01"; -- when in this state the counter increment the
 exit

CONSTANT SRES: STATE_TYPE := "11"; -- when in this state the counter reset the exit

signal s_RPCA : std_logic_vector(N_bitc-1 **downto** 0);

signal retro_add : std_logic_vector(N_bitc-1 **downto** 0);

signal dff_in : std_logic_vector(N_bitc-1 **downto** 0);

signal add_in : std_logic_vector(N_bitc-1 **downto** 0);

signal cout_RPCA : std_logic;

component RPCA **is**

generic(Nbit : integer);

port(

 a : **in** std_logic_vector(Nbit-1 **downto** 0);

 b : **in** std_logic_vector(Nbit-1 **downto** 0);

 cin : **in** std_logic;

 s : **out** std_logic_vector(Nbit-1 **downto** 0);

 cout : **out** std_logic

);

end component;

component DFF **is**

generic(N_bit : integer);

port (

 clk: **in** std_logic;

 reset: **in** std_logic;

 D: **in** std_logic_vector(N_bit-1 **downto** 0);

 Q: **out** std_logic_vector(N_bit-1 **downto** 0)

);

end component;

begin

```

rpca1 : RPCA
generic map(Nbit => N_bitc)
port map(add_in,retro_add,'0',s_RPCA,cout_RPCA);

dff1 : DFF
generic map(N_bit => N_bitc)
port map(count_clk,count_reset,dff_in,retro_add);
counting_proc: process(enabler_in,s_RPCA,count_reset,retro_add)
begin
    add_in<= (N_bitc-1 downto 1 => '0',others => '1');
    if(count_reset='0') then
        dff_in<= (others => '0');
    else
        case(enabler_in) is
        when SMEM=>
            dff_in<=retro_add;
        when SINC=>
            dff_in<=s_RPCA;
        when SRES=>
            dff_in <= (others => '0');
        when others =>
            dff_in <= (others => '0');
        end case;
    end if;
    D_out<=retro_add;
end process;
end Counter_beh;

```

4 Test_benches

Correct sequence Testbench

```
library IEEE;
use IEEE.std_logic_1164.all;

entity SSR_tb is
end SSR_tb;

architecture SSR_tb_beh of SSR_tb is

    constant T_CLK : time := 10 ns; -- Clock period
    constant T_RESET : time := 21 ns; -- Period before the reset deassertion
    constant T_FIRST : time := 13 ns; -- Period before the reset deassertion

    signal clk_tb : std_logic := '0'; -- clock signal, intialized to '0'
    signal rst_tb : std_logic := '0'; -- reset signal
    signal in_tb : std_logic_vector(7 downto 0);
    signal f_tb : std_logic := '0';
    signal out_tb : std_logic;
    signal warn_tb : std_logic;

    component SecureSequenceRec is
        port (
            clock: in std_logic; --- clock signal
            reset: in std_logic; -- reset signal active low
            first: in std_logic; -- start sampling signal
            num_in: in std_logic_vector(7 downto 0); --input sequence number

            unlock: out std_logic; -- signal of success
            warning: out std_logic -- error signal
        );
    end component;

begin

    clk_tb <= not(clk_tb) after T_CLK / 2;
    rst_tb <= '1' after T_RESET; -- Deasserting the reset after T_RESET nanosecods.

    SSR_test: SecureSequenceRec
    port map(clk_tb,rst_tb,f_tb,in_tb,out_tb,warn_tb);

    r_process: process
    begin
        wait for T_RESET;
        in_tb <= "00100100";
        wait for T_FIRST;
        f_tb <= '1';
        wait for T_CLK;
        f_tb <= '0';
    end process;
end;
```


```

in_tb<="00010011";
wait for T_CLK;
in_tb<="00111000";
wait for T_CLK;
in_tb<="01100101";
wait for T_CLK;
in_tb<="01001001";

```

```
end process;
```

```
end SSR_tb_beh;
```

 

Picture 3: Simulation of a correct Sequence

Wrong sequence Testbench

```
library IEEE;
use IEEE.std_logic_1164.all;

entity SSR_tb is
end SSR_tb;

architecture SSR_tb_beh of SSR_tb is

    constant T_CLK : time := 10 ns; -- Clock period
    constant T_RESET : time := 21 ns; -- Period before the reset deassertion
    constant T_FIRST : time := 13 ns; -- Period before the reset deassertion

    signal clk_tb : std_logic := '0'; -- clock signal, intialized to '0'
    signal rst_tb : std_logic := '0'; -- reset signal
    signal in_tb : std_logic_vector(7 downto 0);
    signal f_tb : std_logic := '0';
    signal out_tb : std_logic;
    signal warn_tb : std_logic;

    component SecureSequenceRec is
        port (
            clock: in std_logic; --- clock signal
            reset: in std_logic; -- reset signal active low
            first: in std_logic; -- start sampling signal
            num_in: in std_logic_vector(7 downto 0); --input sequence number

            unlock: out std_logic; -- signal of success
            warning: out std_logic -- error signal
        );
    end component;

begin

    clk_tb <= not(clk_tb) after T_CLK / 2;
    rst_tb <= '1' after T_RESET; -- Deasserting the reset after T_RESET nanosecods.

    SSR_test: SecureSequenceRec
    port map(clk_tb,rst_tb,f_tb,in_tb,out_tb,warn_tb);

    r_process: process
    begin
        wait for T_RESET;
        in_tb <= "00100100";
        wait for T_FIRST;
        f_tb <= '1';
        wait for T_CLK;
        f_tb <= '0';
        in_tb <= "10010011";
        wait for T_CLK;
        in_tb <= "00111000";
```

```

wait for T_CLK;
in_tb<="01100101";
wait for T_CLK;
in_tb<="01001001";

```

```

end process;

```

```

end SSR_tb_beh;


```



Picture 4: Simulation of a wrong Sequence

5 Synthesis on Vivado

Resource utilization

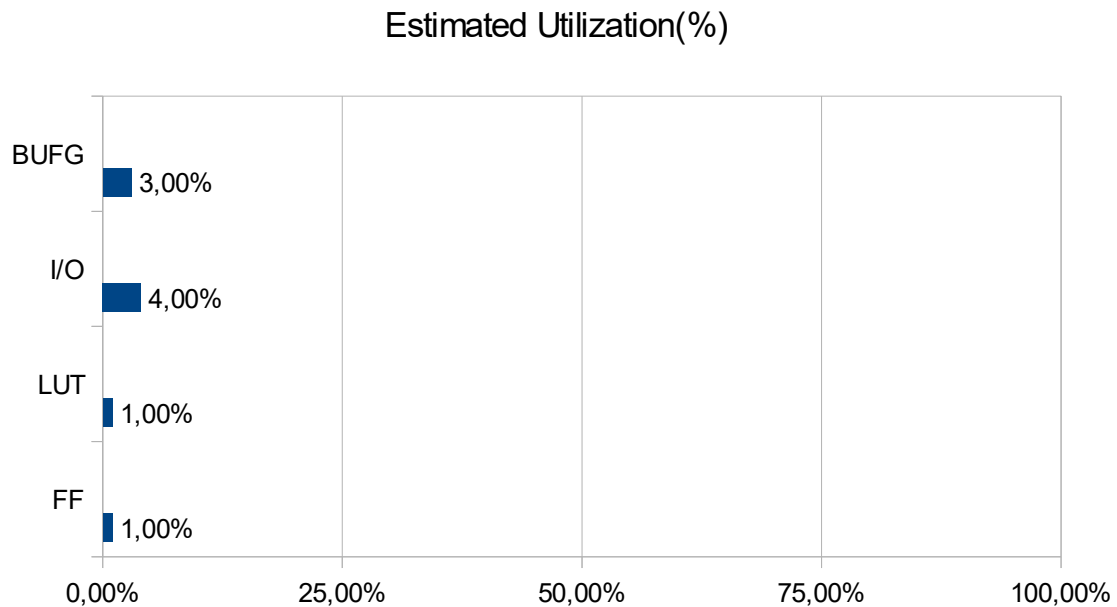

Critical path

Design timing Summary

Setup		Hold		Pulse Width	
Worst Negative Slack	8,333 ns	Worst Hold Slack	0,208 ns	Worst Pulse Width	4,650 ns
Total Negative Slack	0,000 ns	Total Hold Slack	0,000 ns	Total PWS	0,000 ns

Clock Frequency 100 MHz

All user specified timing constraints are met

Warnings

[Synth 8-614] signal 'num_in' is read in the process but is not in the sensitivity list

The sampling must be synchronous with the clock,so just once every clock cycle. Putting the signal in the sensitivity list would have meant corrupting the integrity of the sampling.

[Synth 8-614] signal 'signal_ok_out' is read in the process but is not in the sensitivity list

[Synth 8-614] signal 'count_wr_out' is read in the process but is not in the sensitivity list

[Synth 8-614] signal 'lut_out' is read in the process but is not in the sensitivity list

Those are inner signal used by the SSR ,it would be useless insert them in the sensitivity list